

Total number of printed pages-6

63/1 (SEM-5) SEC3/PHYSE 5032

2023

PHYSICS

Paper : PHYSE 5032

(Electrical Circuits and Network Skills)

Full Marks : 50

Pass Marks : 20

Time : Two hours

The figures in the margin indicate full marks for the questions.

1. Choose the correct answer from the following
(any five) : 1×5=5

(a) The ripple factor of half wave rectifier is

(i) 1.21

(ii) 0.48

(iii) 1.12

(iv) 2.11

(b) A wire of length l is drawn to length $2l$, then its resistance

(i) Increases four times

(ii) Decreases $1/4^{\text{th}}$ of its original length

Contd.

- (iii) Increases two times
 - (iv) Will not change
- (c) A multimeter is an instrument that is used for the measurement of
- (i) Current
 - (ii) Voltage
 - (iii) Resistance
 - (iv) Current, resistance and voltage
- (d) Which type of transformer is required to create a 180° input to the rectifier ?
- (i) Center-tapped secondary
 - (ii) Step-down secondary
 - (iii) Step-up secondary
 - (iv) Split-winding primary
- (e) The total capacitance of 10 capacitors each of value $20 F$ in parallel is
- (i) $100F$
 - (ii) $200F$
 - (iii) $400F$
 - (iv) $300F$
- (f) DC power of an electrical circuit is
- (i) Volt \times Ampere
 - (ii) Volt \times Ohm
 - (iii) Ampere \times Ohm
 - (iv) Volt \times Ampere \times Ohm

- (g) At resonance, the series LCR circuit is equivalent to
- (i) Purely resistive
 - (ii) Purely inductive
 - (iii) Purely capacitive
 - (iv) Purely resistive-inductive
- (h) An electrical motor converts
- (i) Electrical energy to mechanical energy
 - (ii) dc power to ac power
 - (iii) dc current to dc current
 - (iv) None of the above
- (i) A relay is
- (i) Electrical switch
 - (ii) Mechanical switch
 - (iii) Connecting cable
 - (iv) Magnetic switch
- (j) The full form of MCB is
- (i) Miniature contact breaker
 - (ii) Mini circuit breaker
 - (iii) Miniature circuit breaker
 - (iv) Mini contact breaker

2. Answer the following questions (*any five*):
 $2 \times 5 = 10$

- (a) State Ohm's law in electricity. Define resistance.
- (b) State Kirchhoff's law.
- (c) Derive an expression for r.m.s. value of current.
- (d) How can a voltmeter be used to measure the voltage of a cell?
- (e) Find the equivalent capacitance of n -capacitors connected in series.
- (f) Define capacitive reactance and inductive reactance.
- (g) Draw the circuit diagram of a bridge rectifier.

3. Answer the following questions (*any five*):
 $5 \times 5 = 25$

- (a) Derive an expression for equivalent resistance of three resistors connected (i) in series and (ii) in parallel.
 $2\frac{1}{2} + 2\frac{1}{2} = 5$
- (b) Derive an expression for the peak value of current flowing through a series LCR circuit.
 $1 + 4 = 5$

(c) State and prove Thevenin's theorem.
 $1 + 4 = 5$

- (d) Write the steps to convert a given current source into an equivalent voltage source.
- (e) Describe the working of an ac generator with the necessary diagram. $3 + 2 = 5$
- (f) Describe how a Zener diode can be used for voltage regulation.
- (g) What is the Q-factor of an LCR series circuit? Derive an expression for it.
 $1 + 4 = 5$
- (h) Write short notes on different types of electrical drawings and symbols.
- (i) What are the different types of conductors and cables used in electrical wiring? Explain.

4. Answer the following questions (*any one*):
 $10 \times 1 = 10$

- (a) What is a transformer? What are the main types of transformers? Discuss the principle, theory, construction, working and uses of transformer. $1 + 1 + 8 = 10$

(b) What is ripple factor? Derive an expression of ripple factor for (i) half wave rectifier and (ii) full wave rectifier.

2+4+4=10

(c) Explain construction and working of an electric motor with diagram. 5+5=10