

63/1 (SEM-3) CC7/PHYHC3076

2 0 2 2

(Held in 2023)

PHYSICS

Paper : PHYHC3076

(**Digital Systems and Applications**)

Full Marks : 60

Pass Marks : 24

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Choose the correct answer : 1×5=5

(a) The active components in an IC are

(i) diodes

(ii) capacitors

(iii) transistors and diodes

(iv) None of the above

- (b) According to Boolean law, $A + 1 = ?$
- (i) 1
 - (ii) 0
 - (iii) A
 - (iv) \bar{A}
- (c) A decoder converts n inputs to maximum of _____ outputs.
- (i) n
 - (ii) n^2
 - (iii) 2^n
 - (iv) n^{-1}
- (d) How is a J-K flip-flop made to toggle?
- (i) $J = 0, K = 0$
 - (ii) $J = 1, K = 1$
 - (iii) $J = 1, K = 0$
 - (iv) $J = 0, K = 1$
- (e) Assembly language programs are written using
- (i) HEX code
 - (ii) ASCII code
 - (iii) mnemonics
 - (iv) None of the above

2. Answer the following questions : 2×5=10
- (a) What do you mean by rise time of a CRO? How is bandwidth of a CRO related to its rise time? 1+1=2
- (b) In basic IC terminology, what are 'wafer' and 'chip'? Define those. 1+1=2
- (c) Convert the following hexadecimal numbers into binary numbers : 1+1=2
- (i) $(7A \cdot 2C)_{16}$
 - (ii) $(FF8)_{16}$
- (d) What is a multiplexer? Draw the circuit of a 4-1 multiplexer. 1+1=2
- (e) Write the difference between combinational circuits and sequential circuits. 2
3. Answer any *five* of the following questions : 5×5=25
- (a) What is the drawback of J-K flip-flop? How is it overcome in master-slave J-K flip-flop? Explain it with necessary circuit diagram and truth table. 1+4=5
- (b) Describe an astable multivibrator using IC 555. 5
- (c) What do you mean by shift register? What are its different types? Draw the circuit symbol of each type. 1+1+3=5

- (d) Write briefly on the bus structure of microprocessor. 5
- (e) Draw the block diagram of a CRO and label its different parts. What is electron gun? 3+2=5
- (f) What is a ring counter? Describe its construction and working. 1+4=5
- (g) What do you mean by decoder? Describe a 2-4 decoder. 1+4=5

4. Answer any *two* of the following questions :

10×2=20

- (a) What is a K-map? Define pair, quad, octet, redundant groups with examples in K-map. 1+9=10
- (b) Write short notes on any *two* of the following : 5×2=10
- (i) Computer memory
 - (ii) Assembly language
 - (iii) Full-adder
- (c) (i) Realize two-input NAND and NOR gates with diodes and transistors. Write their truth tables. 1+1+1+2=5
- (ii) What do you mean by parity? Write its importance in digital electronics. What are its different types? 1+2+2=5

★ ★ ★