

Total number of printed pages-9

63/1 (SEM-4) CC10/PHYHC4106

2025

PHYSICS

Paper : PHYHC4106

(Analog Systems and Applications)

Full Marks : 60

Pass Marks : 24

Time : Three hours

The figures in the margin indicate full marks for the questions.

1. Choose the correct answer for following questions : **(any five)** 1×5=5
- (a) Depletion region is a zone that contains
- (i) electrons only
 - (ii) holes only
 - (iii) ions only
 - (iv) both electrons and holes

(b) In a transistor biased in common emitter mode, the emitter current is

- (i) nearly equal to the base current
- (ii) much larger than base current
- (iii) much smaller than the collector current
- (iv) much smaller than the base current

(c) The ripple factor of a bridge rectifier is

- (i) 1.21 (ii) 0.812
- (iii) 0.482 (iv) 0.406

(d) The Voltage divider circuit is used in amplifiers, because it

- (i) limits the ac signal going to the base
- (ii) reduces the base current
- (iii) makes the operating point independent of β
- (iv) makes the circuit simple

(e) A multistage amplifier has two stages. The voltage gains of the stages are 10 and 20 respectively. Overall gain of the amplifier is

- (i) 100 (ii) 150
- (iii) 200 (iv) 250

(f) By introducing negative feedback in an amplifier there is increase in

- (i) noise level
- (ii) bandwidth
- (iii) harmonic distortion
- (iv) voltage gain

(g) An oscillator differs from an amplifier because it

- (i) has more gain
- (ii) requires no input signal
- (iii) requires no d.c. supply
- (iv) always has same input

(h) With zero volts on both the inputs, an ideal OPAM should have an output

- (i) equal to CMRR
- (ii) equal to the positive supply voltage
- (iii) equal to the negative supply voltage
- (iv) equal to zero

(i) The input stage of an OPAM is usually

- (i) a differential amplifier
- (ii) an integrator
- (iii) CE amplifier
- (iv) common mode amplifier

(j) The most popular type of DAC (Digital to Analog Converter) is

- (i) R-2R ladder type
- (ii) weighted resistor type
- (iii) switch current source type
- (iv) switch capacitor type

2. Answer **any five** of the following questions :

$$2 \times 5 = 10$$


- (a) Mention two differences between a photo-diode and solar cell.
- (b) For a transistor, define DC load line and operating point. $1+1=2$
- (c) Sketch a neat circuit diagram of a RC phase-shift oscillator. How is the positive feedback realized in this oscillator ? $1+1=2$
- (d) Explain the concept of virtual ground in case of OPAM.
- (e) An OPAM has a slew rate of $0.5 \text{ V}/\mu\text{s}$ and peak output voltage of 100 mV . What is the maximum operating frequency of the OPAM ?
- (f) How will you use an OPAM as an inverting adder ?
- (g) What is an ADC ?

3. Answer the following questions : (**any five**)

$$5 \times 5 = 25$$

- (a) What are extrinsic and intrinsic semiconductors ? How are n -type and p -type semiconductors prepared ? $2+(1\frac{1}{2}+1\frac{1}{2})=5$
- (b) Draw the circuit diagram of a full-wave rectifier and explain its operation. Obtain an expression for its rectification efficiency. $3+2=5$
- (c) Draw the circuits in common emitter, common base and common collector configurations for an NPN transistor with proper bias. A transistor is connected in common base configuration. If $I_C = 1.9 \text{ mA}$ and $I_B = 0.05 \text{ mA}$, find the current amplification factor in common base and common emitter connection of this transistor. $3+2=5$
- (d) What are active region, situation region, and cut-off region in transistor operation ? Mark these regions in a diagram of output characteristics of common emitter transistor configuration. $3+2=5$
- (e) Draw the circuit diagram of a Hartley oscillator and explain its operation.

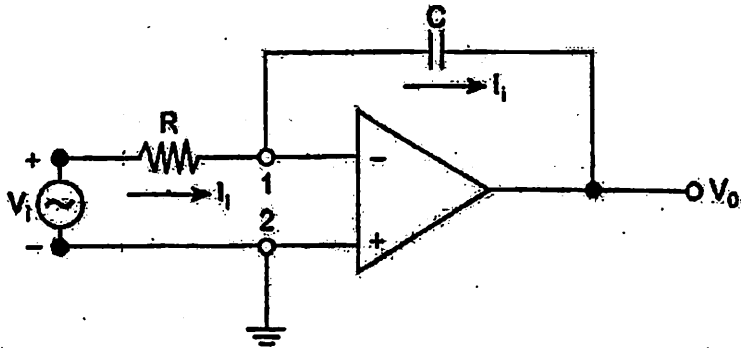(f) In the following circuit, show that the output voltage is the integral of input voltage :



If a sinusoidal voltage $V_i = 10 \sin 2000 \pi t \text{ mV}$ is applied to the input of an OPAM as a differentiator with $C = 1 \mu\text{F}$ and $R = 100 \text{ k}\Omega$, what would be the output voltage ? 3+2=5

(g) Write a short note on either 'Zero Crossing Detector' or 'Wien Bridge Oscillator'.

(h) Explain mathematically why the gain of a RC-coupled amplifier decreases in low frequency region.

(i) Write down two advantages of negative feedback in an amplifier ? A transistor amplifier has a voltage gain of 100. The input resistance of the amplifier is $10 \text{ k}\Omega$ and the output resistance is 100Ω . The amplifier is provided with negative feedback with feedback fraction 0.1. Calculate the voltage gain, input resistance and output resistance after application of negative feedback.

2+3=5

4. Answer **any two** of (a), (b), (c) and (d) :

$10 \times 2 = 20$

(a) (i) Explain the working principle of an LED. Mention two advantages of LED lamps over conventional lamps. The band gap of Gallium Phosphide is 2.26 eV . Determine the wavelength and colour emitted by an LED made of this material.

2+2+2=6

(ii) Explain how stability is achieved in voltage divider bias with a proper circuit diagram.

4

(b) Draw the block diagram of a two-port four-terminal network and mention the voltage and current equations assuming a hybrid parameter model. Draw hybrid parameter equivalent model of a transistor in common emitter configuration and derive the expressions for its current gain, input impedance and voltage gain. $2+(2+2+2+2)=10$

(c) (i) Draw the frequency response curve of a two-stage RC-coupled amplifier clearly showing the half power frequencies and width. Mention one advantage and one disadvantage of a RC-coupled amplifier. $2+2=4$

(ii) Obtain the expression of voltage gain of an amplifier with positive feedback including proper block diagram. What is return difference? $3+1=4$

(iii) Find the operating frequency of a Colpitts Oscillator if $C_1 = 0.001 \mu\text{F}$, $C_2 = 0.01 \mu\text{F}$ and $L = 15 \mu\text{H}$. 2

(d) (i) Explain the working of $p-n$ junction in forward biased condition. Draw its V-I characteristics curve. What are static and dynamic resistances? $3+1+2=6$

(ii) Define mobility of a charge carrier. Obtain the conductivity expression for an extrinsic semiconductor. $2+2=4$
